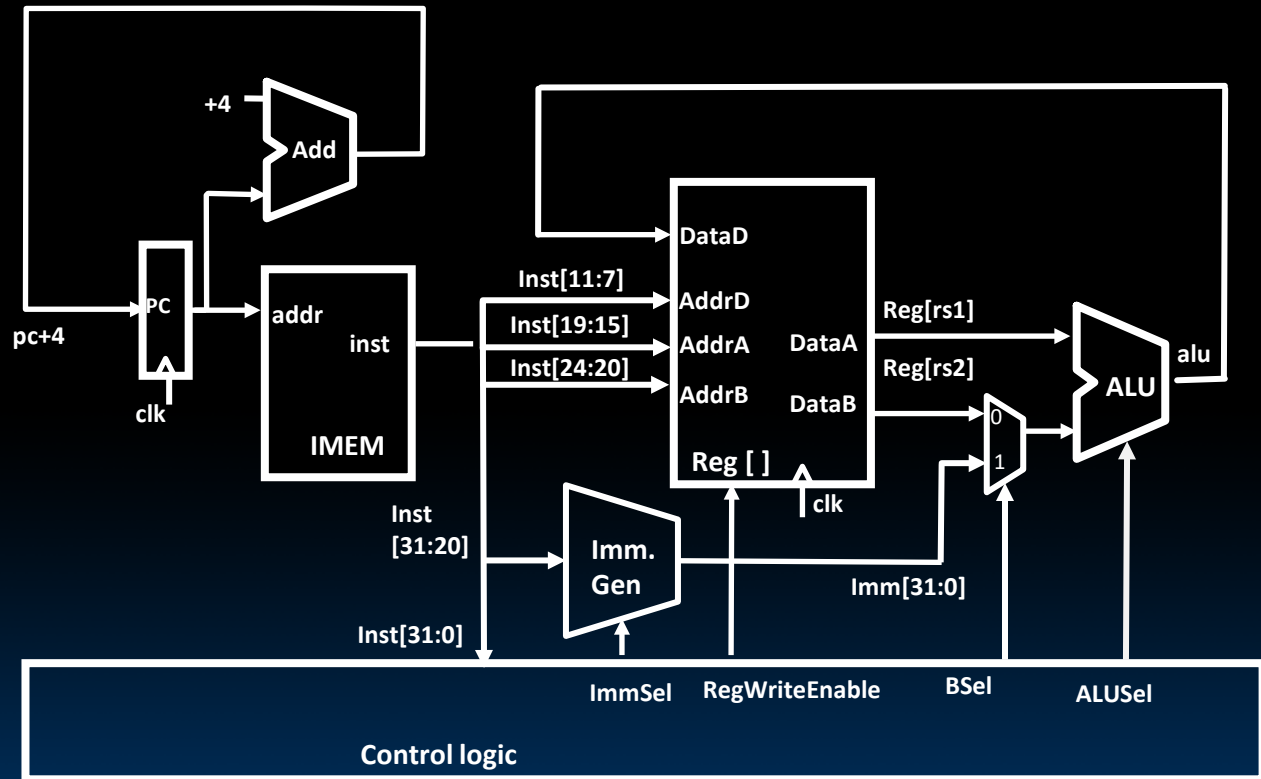



Supporting Loads

R+I Arithmetic/Logic Datapath




Add lw

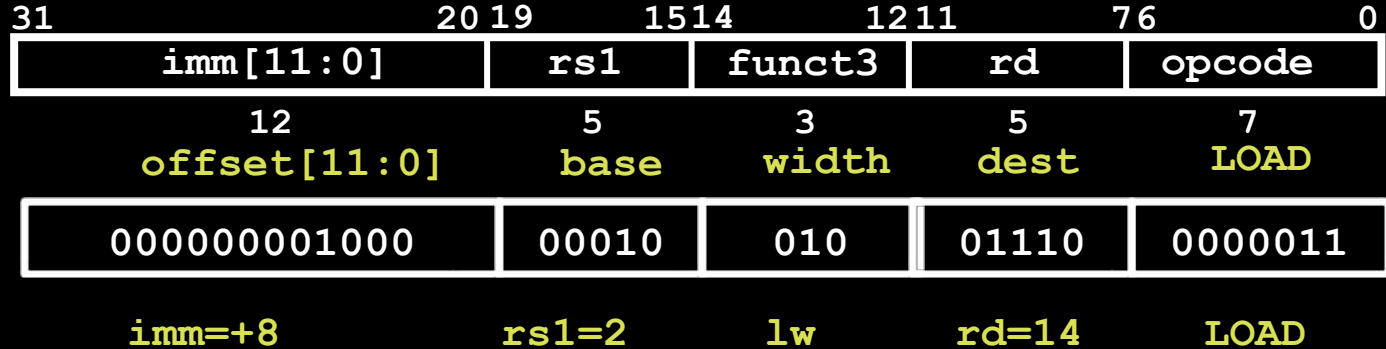- RISC-V Assembly Instruction (I-type): **lw x14, 8(x2)**




- The 12-bit signed immediate is added to the base address in register **rs1** to form the **memory** address
 - This is very similar to the add-immediate operation but used to create address not to create final result
- The value loaded from **memory** is stored in register **rd**

R+I Arithmetic/Logic Datapath

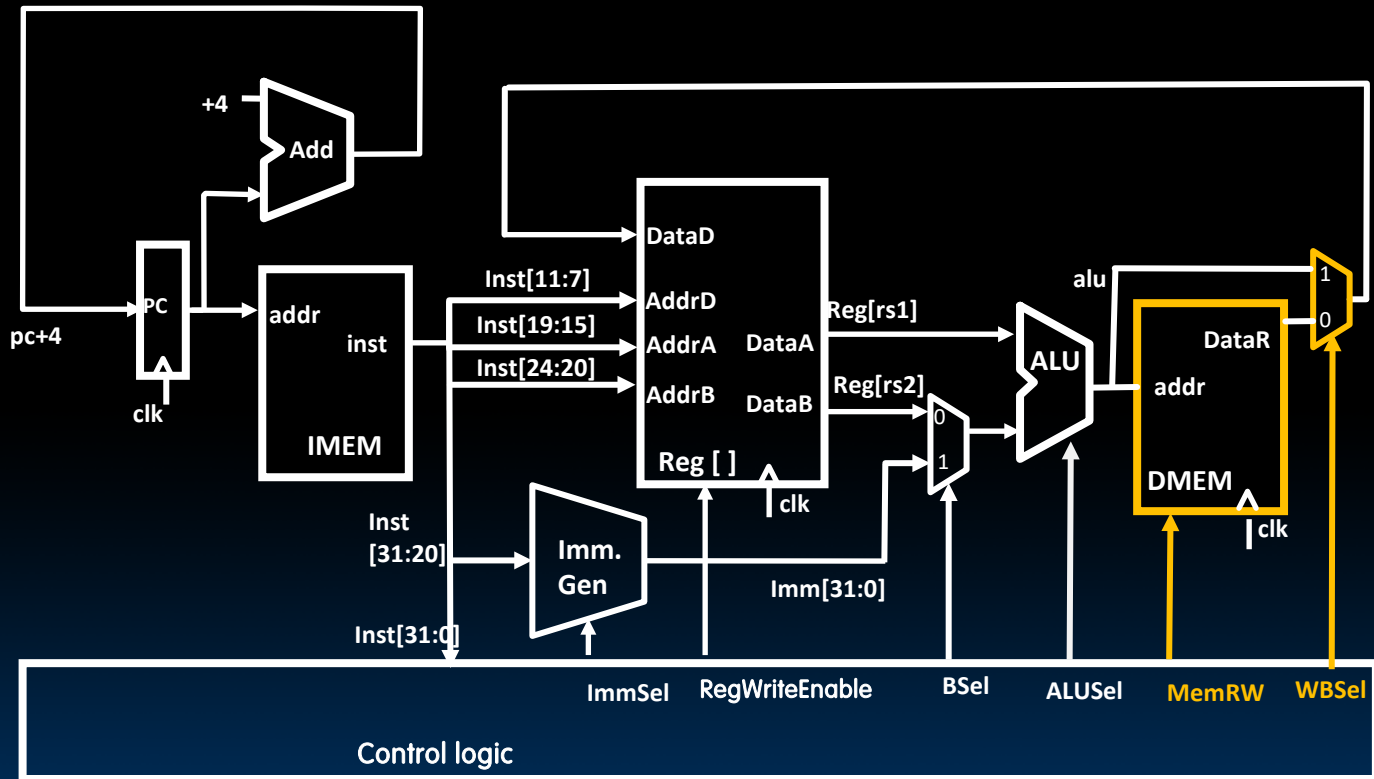

R+I Arithmetic/Logic Datapath

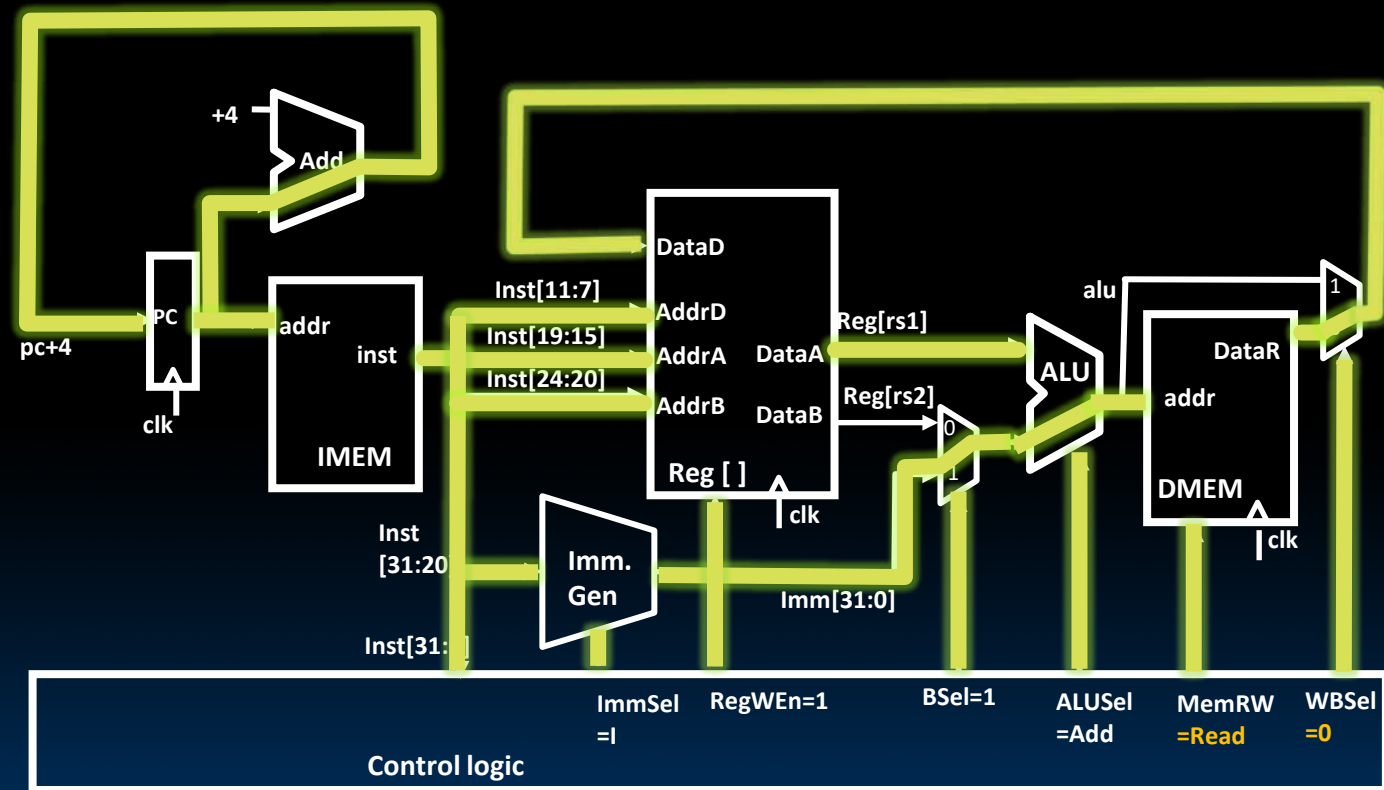

All RV32 Load Instructions

<code>imm[11:0]</code>	<code>rs1</code>	<code>000</code>	<code>rd</code>	<code>0000011</code>	lb
<code>imm[11:0]</code>	<code>rs1</code>	<code>001</code>	<code>rd</code>	<code>0000011</code>	lh
<code>imm[11:0]</code>	<code>rs1</code>	<code>010</code>	<code>rd</code>	<code>0000011</code>	lw
<code>imm[11:0]</code>	<code>rs1</code>	<code>100</code>	<code>rd</code>	<code>0000011</code>	lbu
<code>imm[11:0]</code>	<code>rs1</code>	<code>101</code>	<code>rd</code>	<code>0000011</code>	lhu

↑ funct3 field encodes size and 'signedness' of load data



- Supporting the narrower loads requires additional logic to extract the correct byte/halfword from the value loaded from memory, and sign- or zero-extend the result to 32 bits before writing back to register file.
 - It is just a mux + a few gates

Datapath for Stores


Adding sw instruction

- **sw**: Reads two registers, rs1 for base memory address, and rs2 for data to be stored, as well immediate offset!


sw x14, 8(x2)

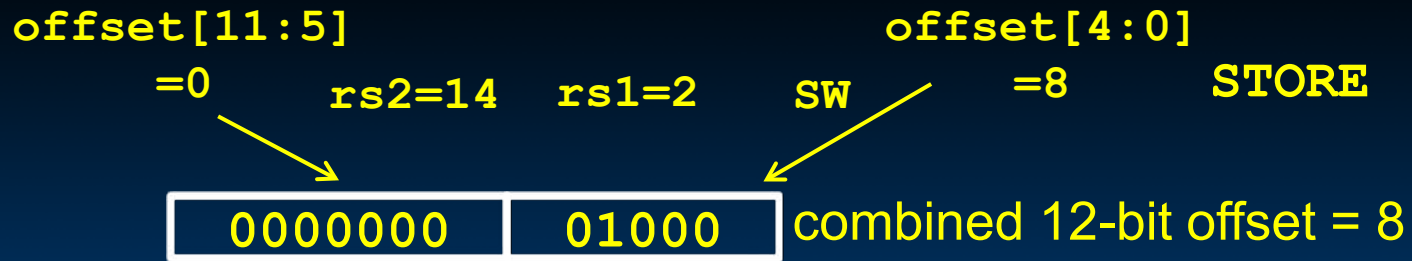 


Datapath with 1w

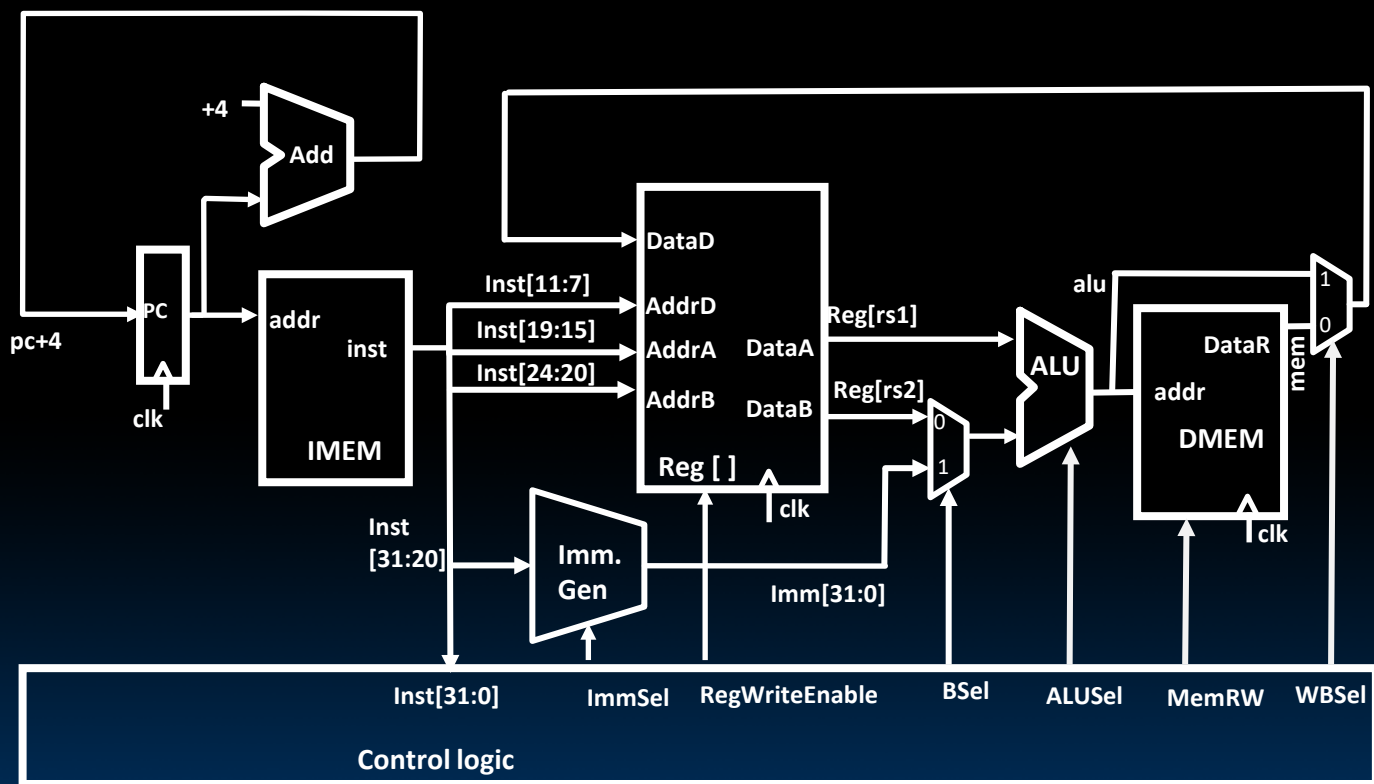


Adding sw to Datapath

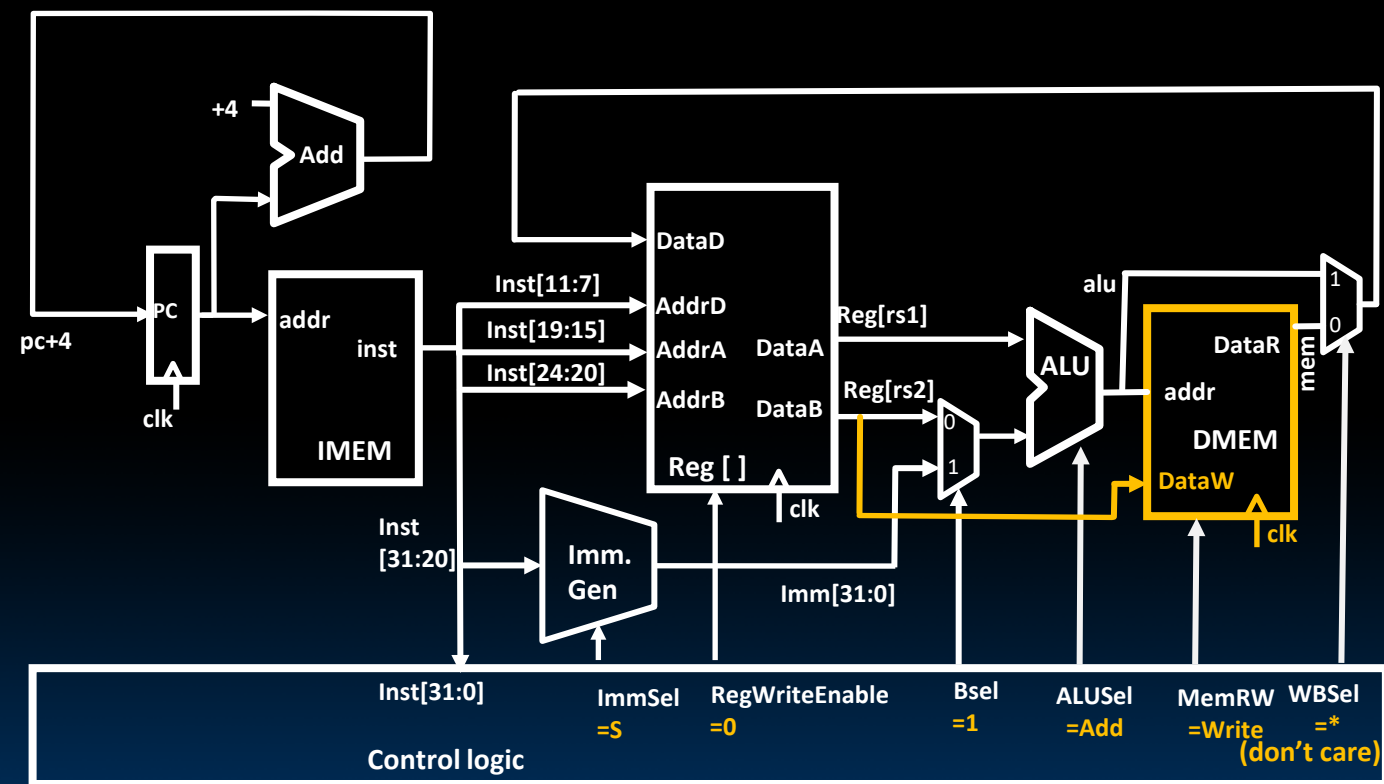

Adding sw to Datapath

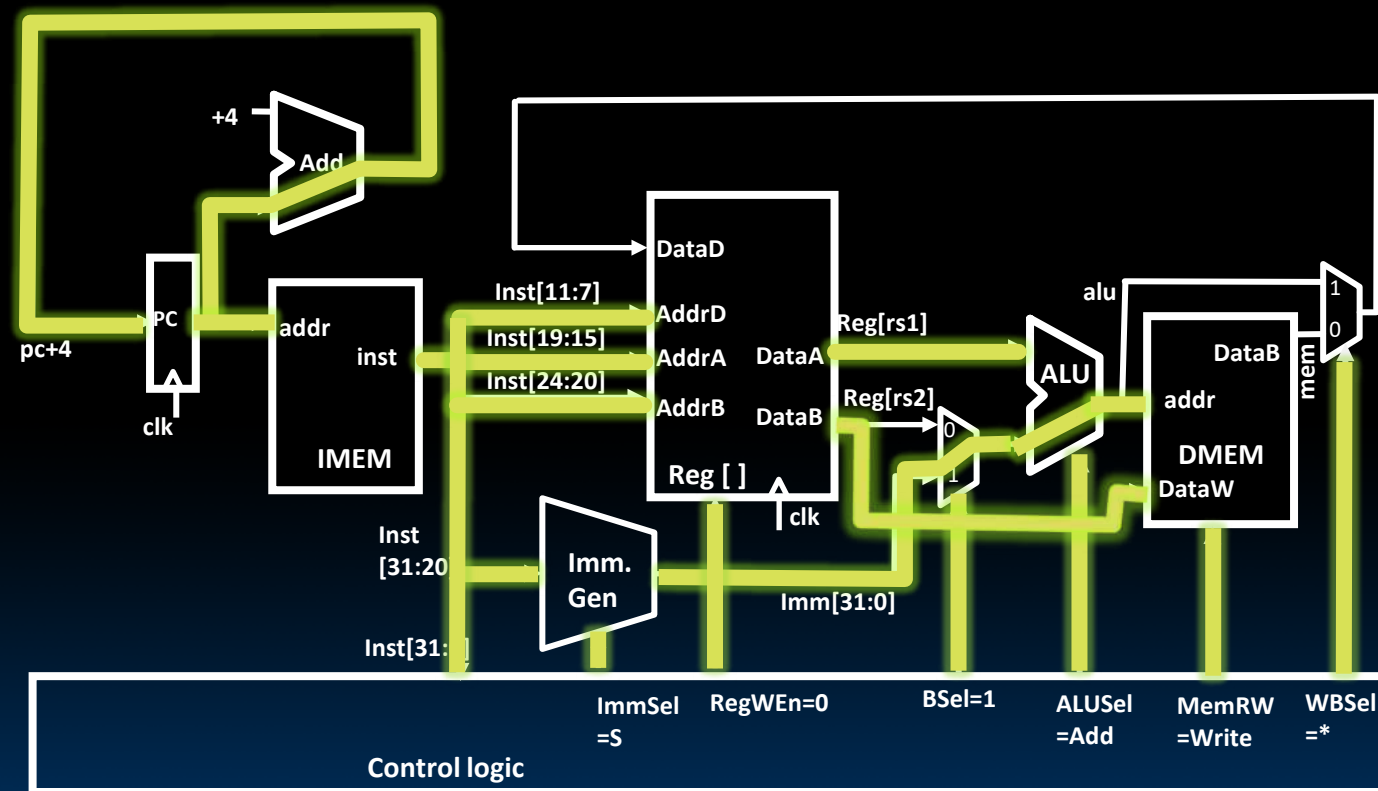

I+S Immediate Generation

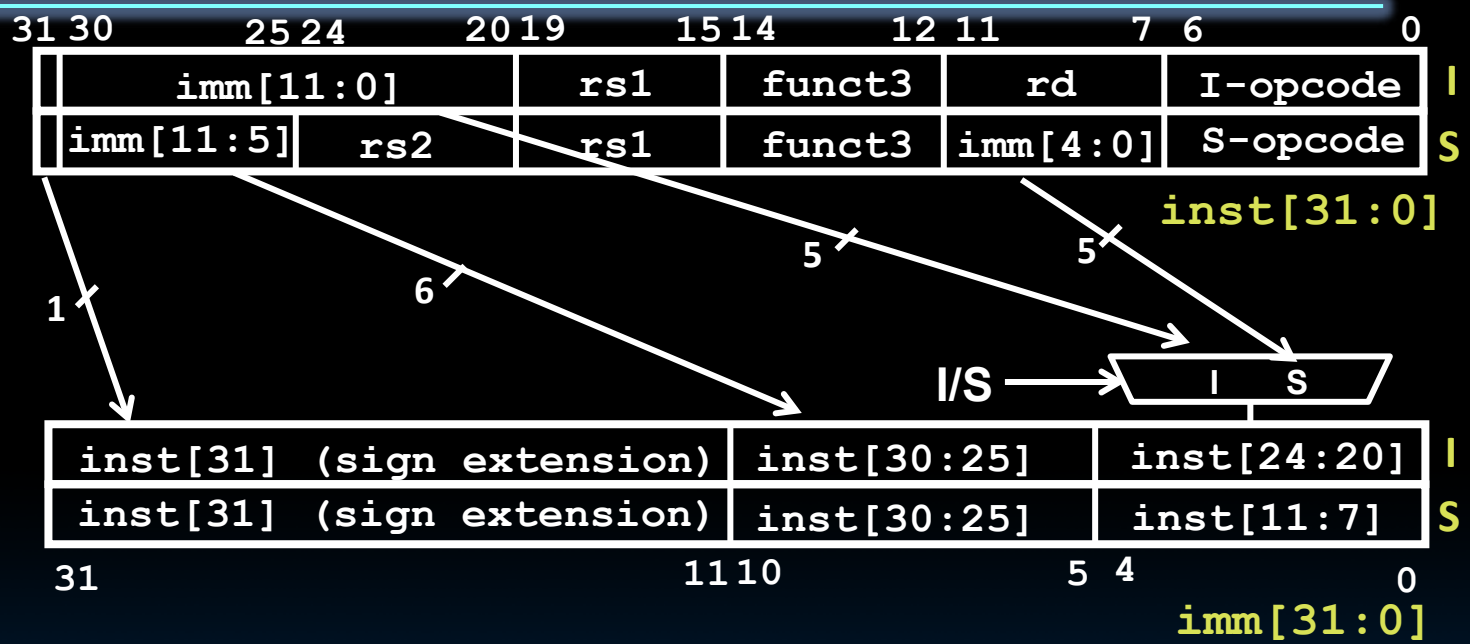

- Just need a 5-bit mux to select between two positions where low five bits of immediate can reside in instruction
- Other bits in immediate are wired to fixed positions in instruction

All RV32 Store Instructions


- Store byte writes the low byte to memory
- Store halfword writes the lower two bytes to memory

Imm[11:5]	rs2	rs1	000	imm[4:0]	0100011	sb
Imm[11:5]	rs2	rs1	001	imm[4:0]	0100011	sh
Imm[11:5]	rs2	rs1	010	imm[4:0]	0100011	sw

width


Implementing Branches

RISC-V B-Format for Branches

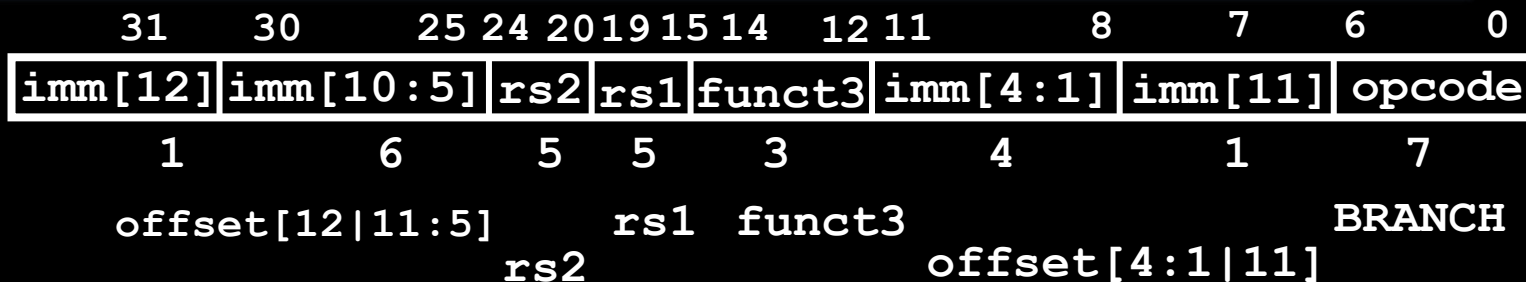

- B-format is mostly same as S-Format, with two register sources (**rs1/rs2**) and a 12-bit immediate **imm[12:1]**
- But now immediate represents values -4096 to +4094 in 2-byte increments
- The 12 immediate bits encode **even** 13-bit signed byte offsets (lowest bit of offset is always zero, so no need to store it)


Datapath So Far

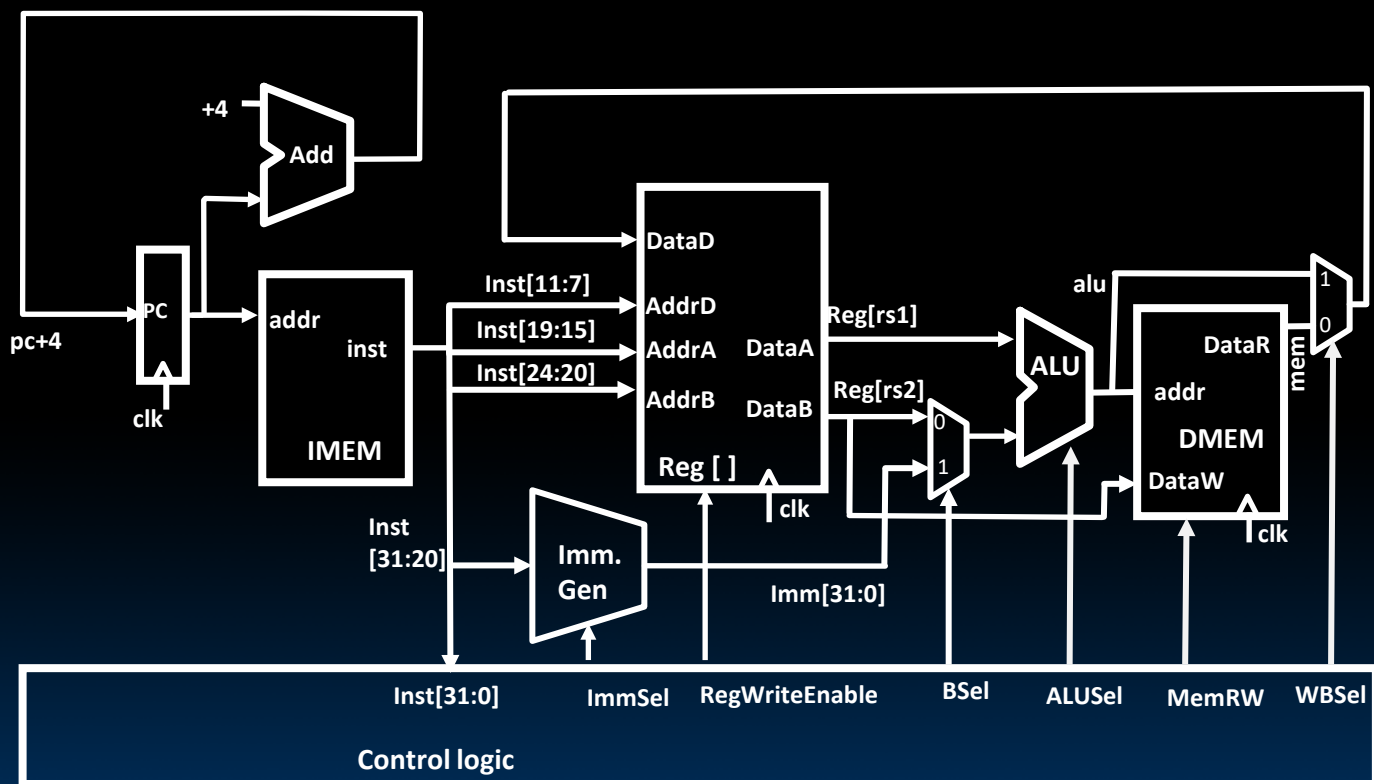


To Add Branches

- Different change to the state:
$$PC = \begin{cases} PC + 4, & \text{branch not taken} \\ PC + \text{immediate}, & \text{branch taken} \end{cases}$$
- Six branch instructions: **beq**, **bne**, **blt**, **bge**, **bltu**, **bgeu**
- Need to compute **PC + immediate** and to compare values of **rs1** and **rs2**
 - But have only one ALU – need more hardware

Adding Branches

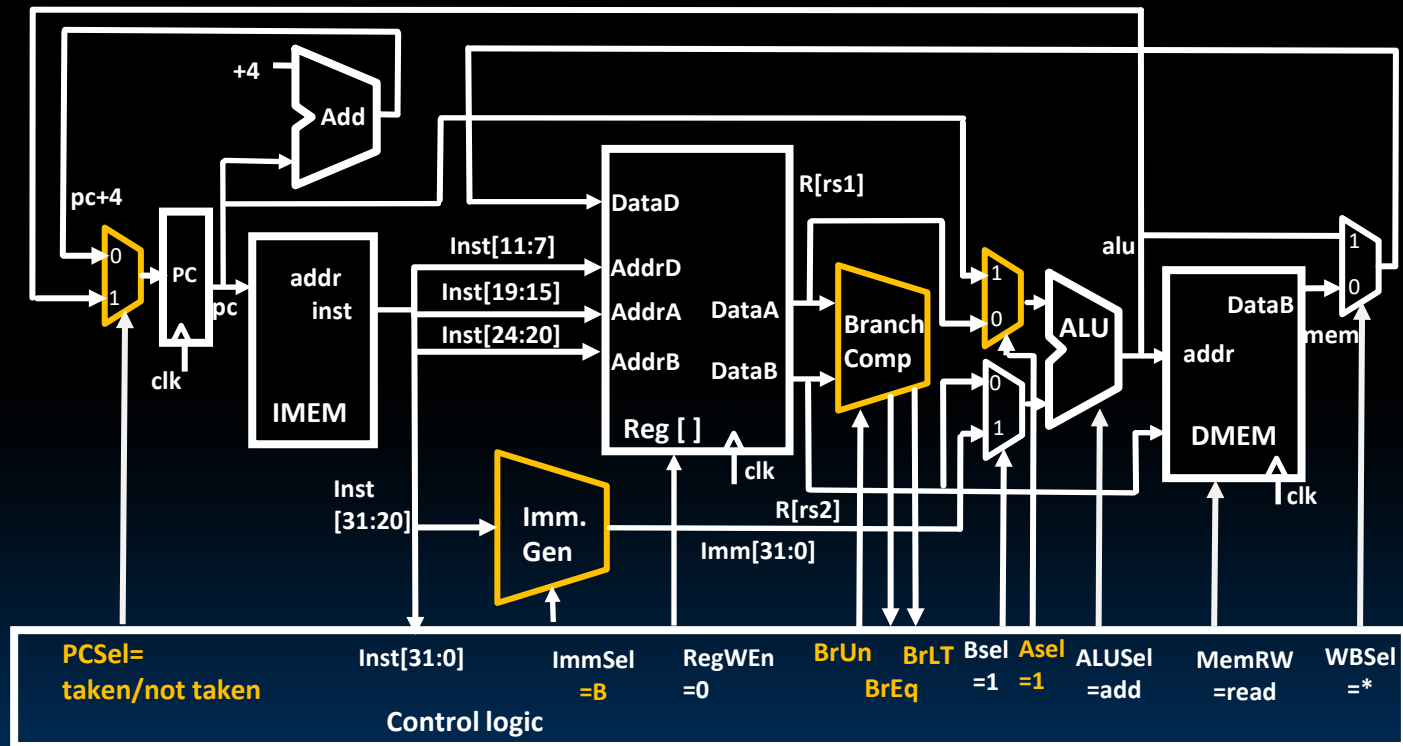

Branch Comparator

 

$\text{BrEq} = 1, \text{ if } A=B$

$\text{BrLT} = 1, \text{ if } A<B$

$\text{BrUn} = 1$ selects unsigned comparison for BrLT ,
0=signed


$\overline{\text{BGE}}$ branch: $A \geq B$, if $\overline{A<B}$

$\overline{A<B} = \neg(A<B)$

Branch Immediates (In Other ISAs)

12-bit immediate encodes PC-relative offset of -4096 to +4094 bytes in multiples of 2 bytes

 Standard approach: Treat immediate as in range -2048..+2047, then shift left by 1 bit to multiply by 2 for branches



Each instruction immediate bit can appear in one of two places in output immediate value – so need one 2-way mux per bit

Branch Immediates (In Other ISAs)

12-bit immediate encodes PC-relative offset of -4096 to +4094 bytes in multiples of 2 bytes

RISC-V approach: keep 11 immediate bits in fixed position in output value

<code>sign=imm[11]</code>	<code>imm[10:5]</code>	<code>imm[4:0]</code>
---------------------------	------------------------	-----------------------

S-Immediate

<code>sign=imm[12]</code>	<code>imm[11]</code>	<code>imm[10:5]</code>	<code>imm[4:1]</code>	<code>0</code>
---------------------------	----------------------	------------------------	-----------------------	----------------

B-Immediate
(shift left by 1)

Only one bit changes position between S and B, so only need a single-bit 2-way mux

RISC-V Immediate Encoding

Instruction encodings, inst[31:0]

31	30	25	24	20	19	15	14	12	11	8	7	6	0		
imm[11:0]					rs1		funct3		rd			opcode		I-type	
imm[11:5]				rs2		rs1		funct3		imm[4:0]			opcode		S-type
imm[12 10:5]				rs2		rs1		funct3		imm[4:1 11]			opcode		B-type


32-bit immediates produced, imm[31:0]

31	25	24	12	11	10	5	4	1	0			
-inst[31]-					inst[30:25]		inst[24:21]		inst[20]		I-imm.	
-inst[31]-					inst[30:25]		inst[11:8]		inst[7]		S-imm.	
-inst[31]-				inst[7]		inst[30:25]		inst[11:8]		0		B-imm.

Upper bits sign-extended from inst[31] always


Only bit 7 of instruction changes role in immediate between S and B

Lighting Up Branch Path

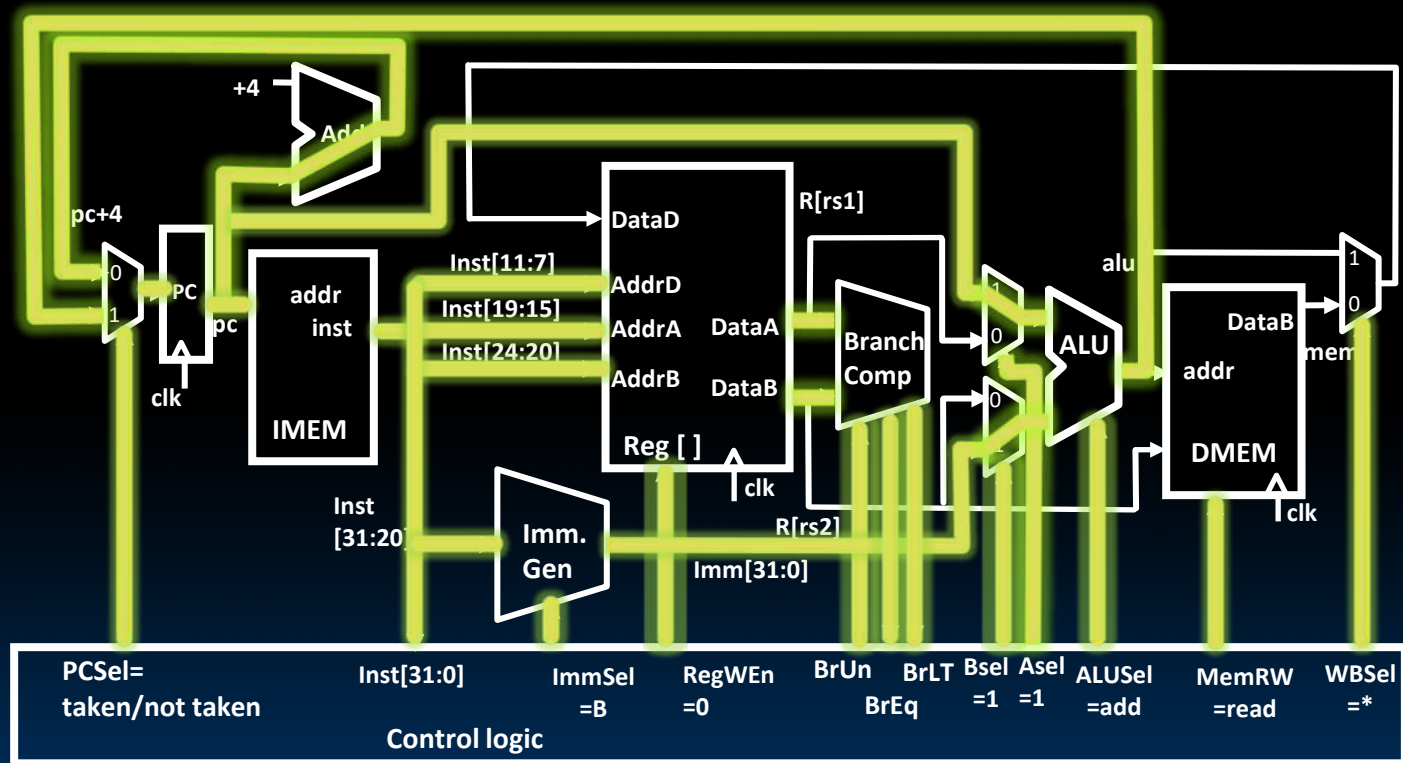


Adding JALR to Datapath

Let's Add JALR (I-Format)

 


- JALR rd, rs, immediate
- Two changes to the state
 - Writes PC+4 to **rd** (return address)
 - Sets PC = **rs1** + **immediate**
 - Uses same immediates as arithmetic and loads
 - **no** multiplication by 2 bytes
 - LSB is ignored


Datapath So Far, With Branches

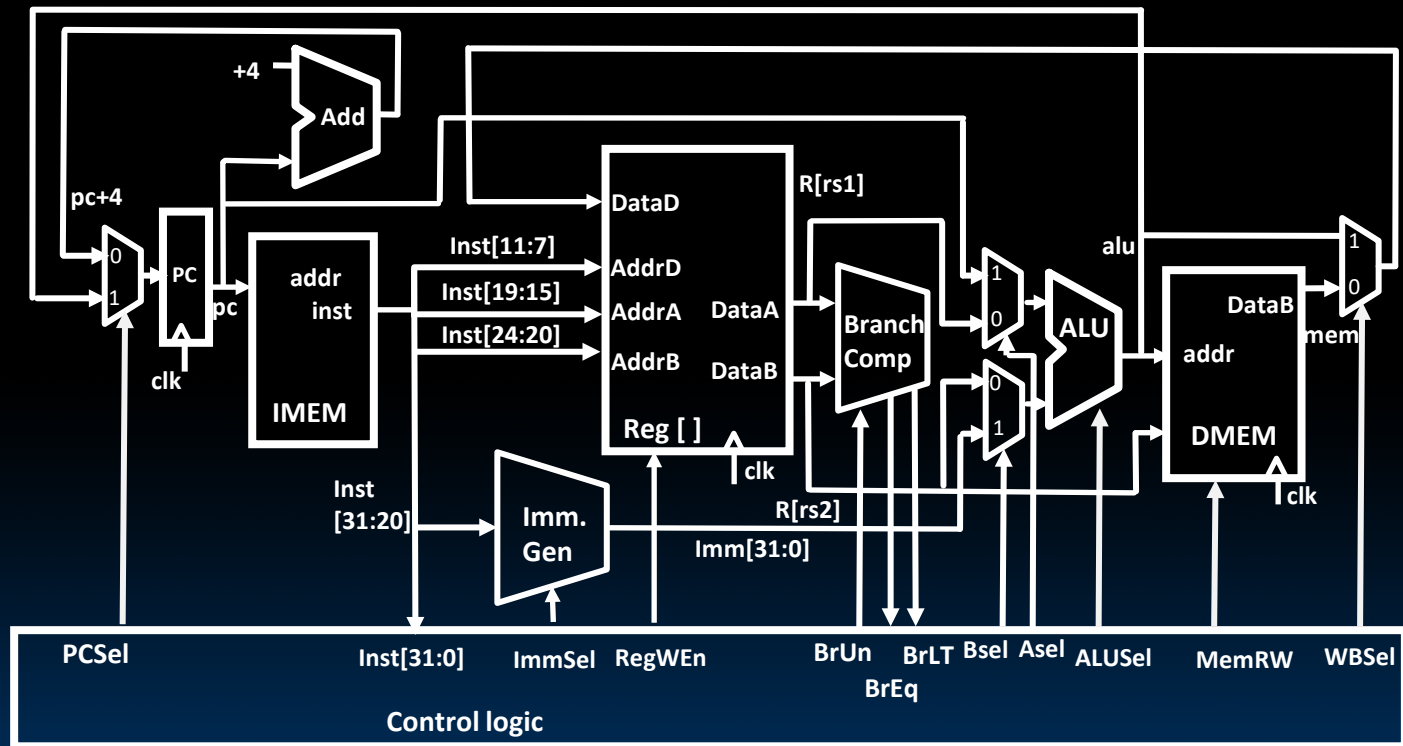

Datapath With JALR

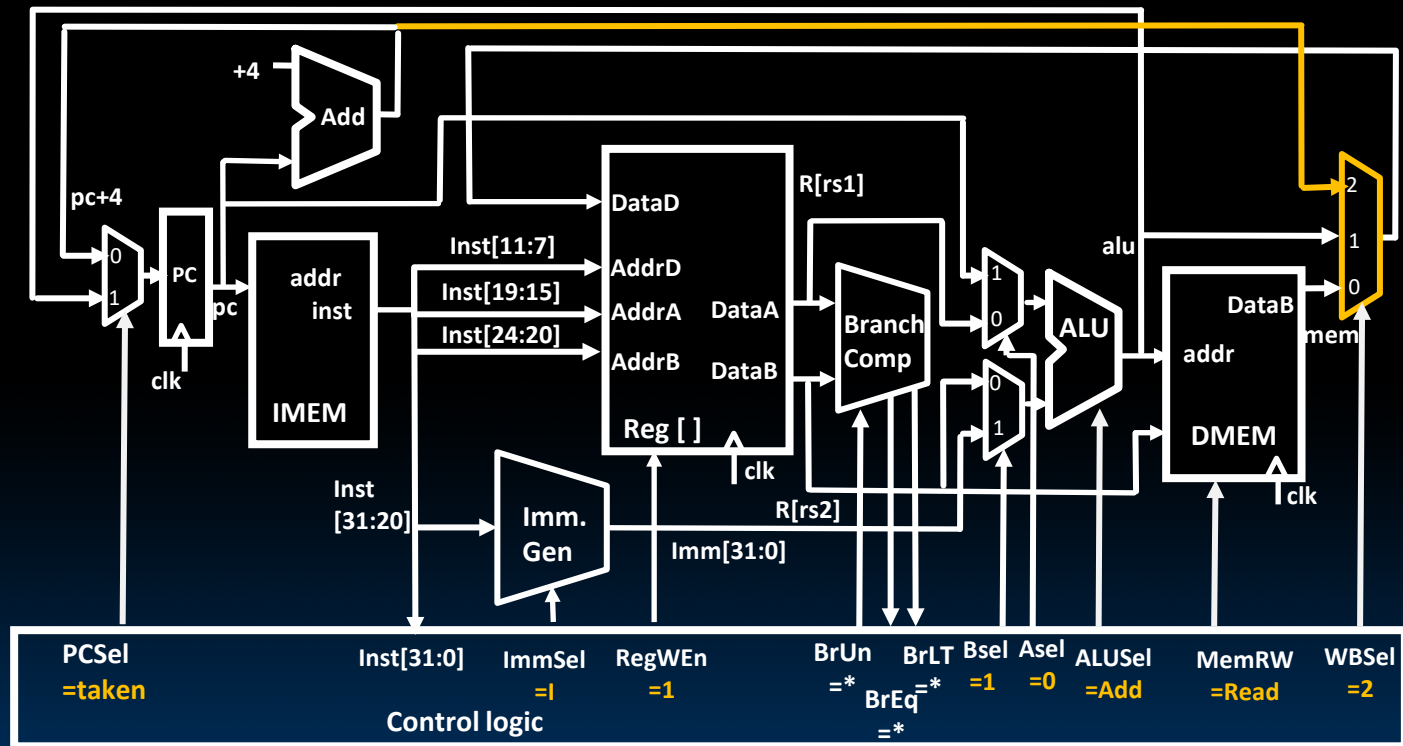


Datapath With JALR

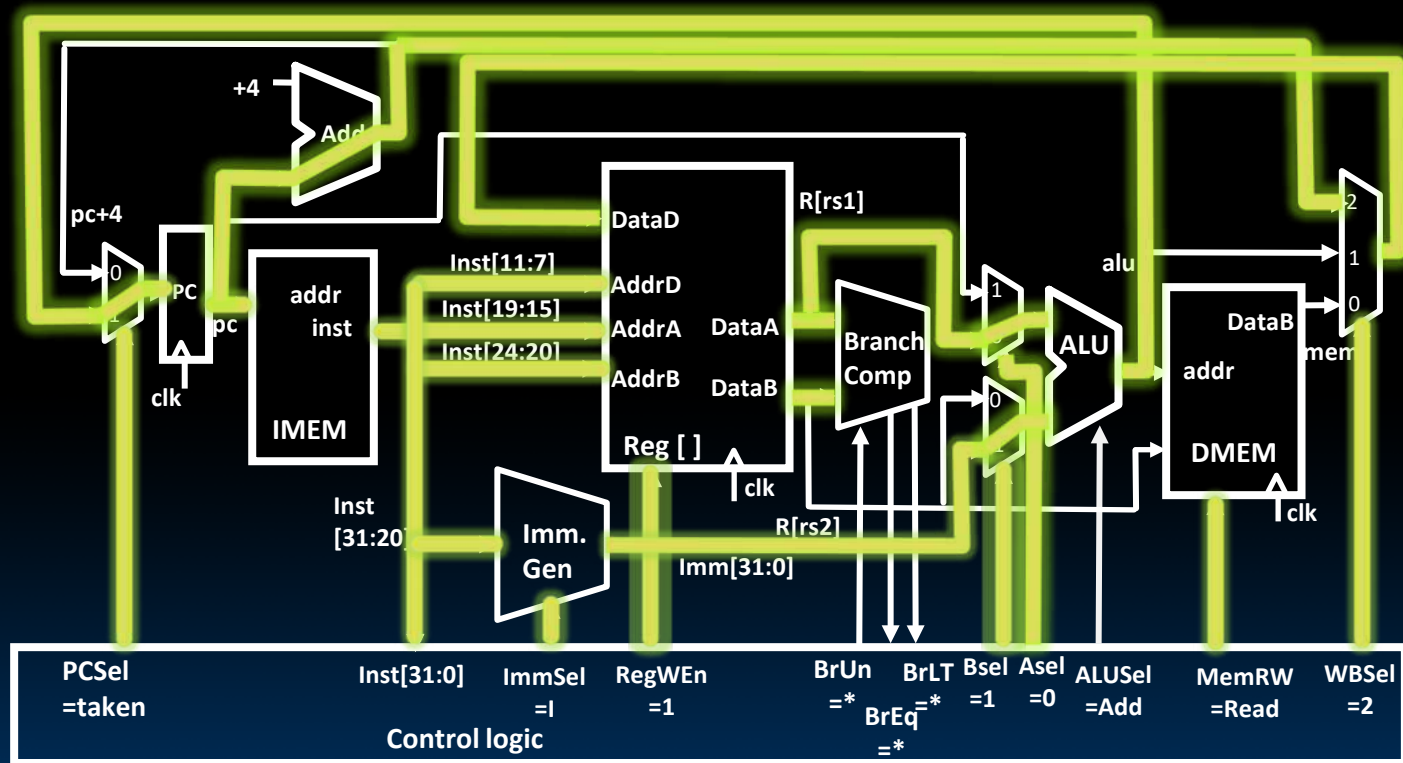


Adding JAL

J-Format for Jump Instructions

 


- Two changes to the state
 - `jal` saves PC+4 in register `rd` (the return address)
 - Set PC = PC + offset (PC-relative jump)
- Target somewhere within $\pm 2^{19}$ locations, 2 bytes apart
 - $\pm 2^{18}$ 32-bit instructions
- Immediate encoding optimized similarly to branch instruction to reduce hardware cost

Datapath with JAL

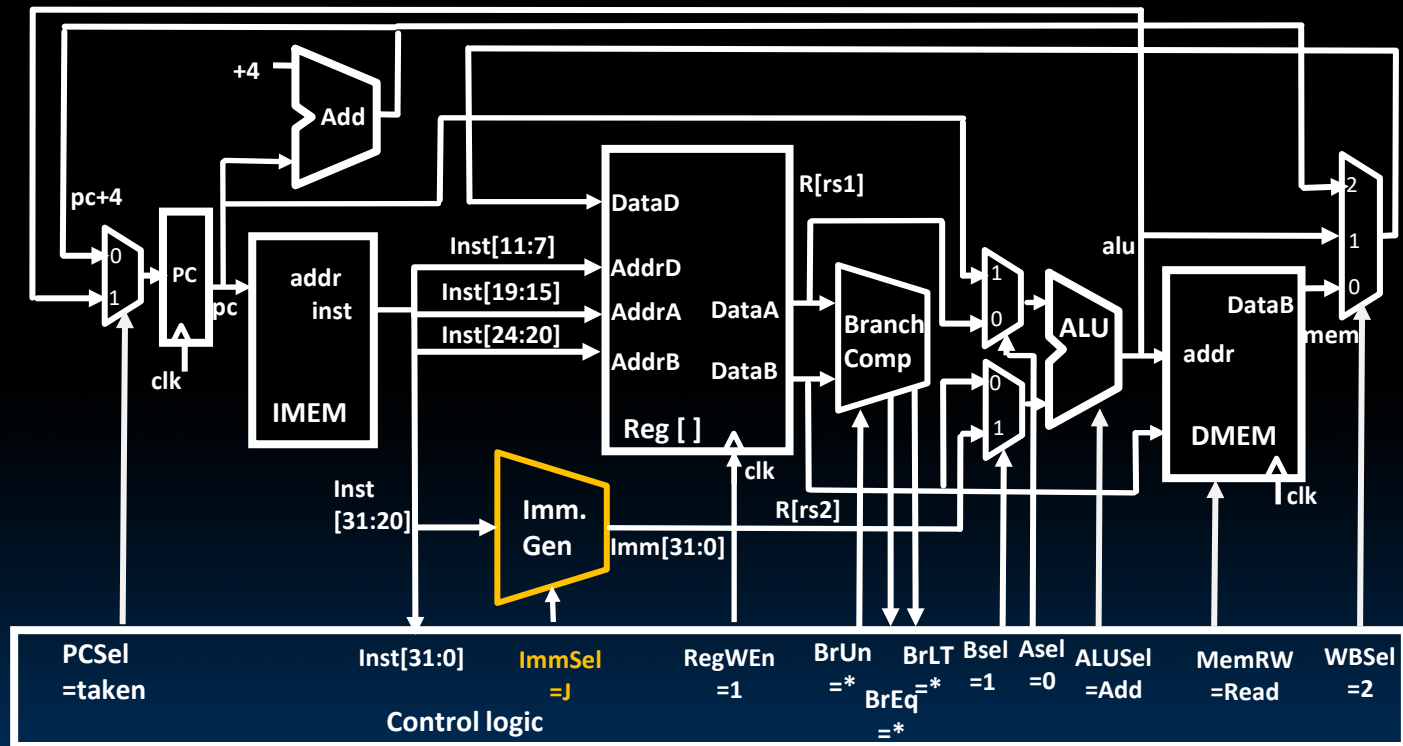


Light Up JAL Path

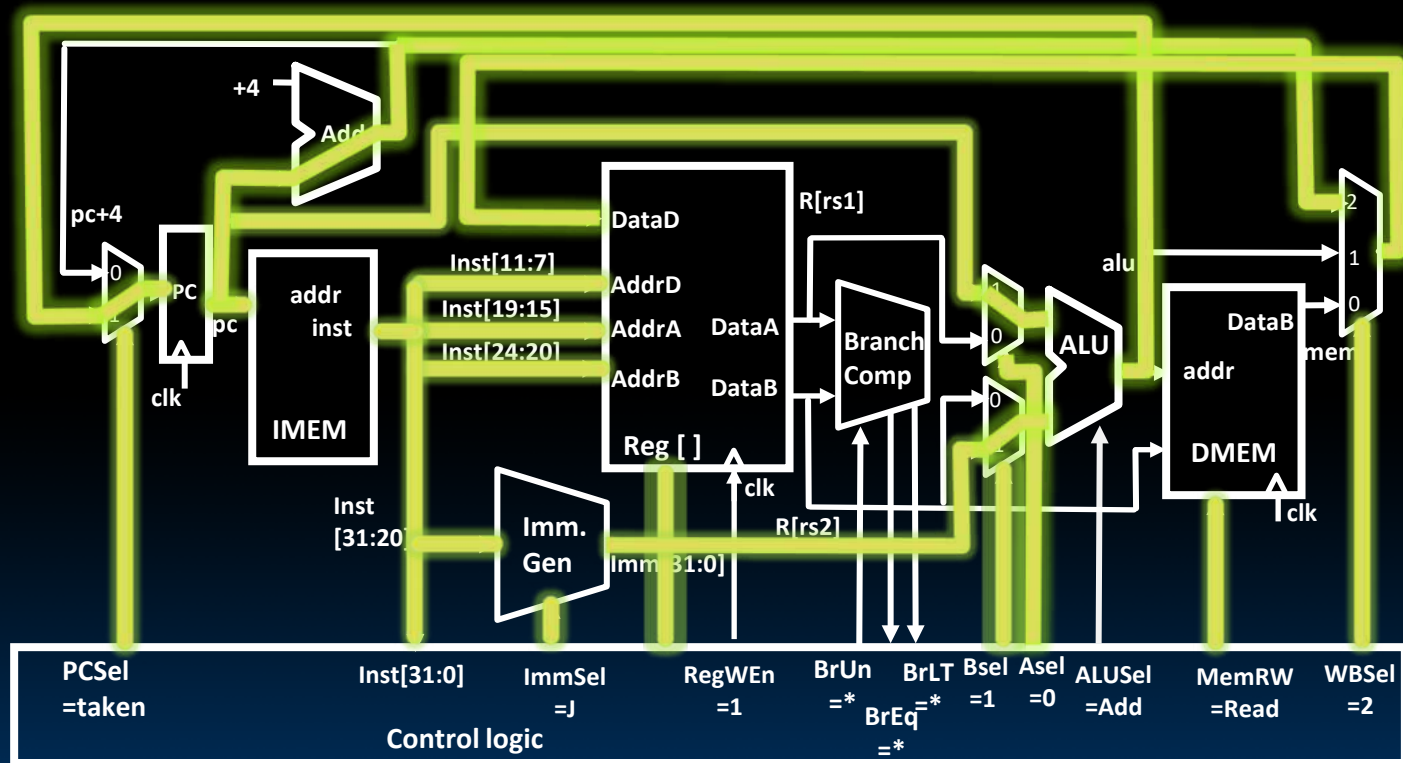

Adding U-Types

 
U-Format for “Upper Immediate” Instructions




- Has 20-bit immediate in upper 20 bits of 32-bit instruction word
- One destination register, **rd**
- Used for two instructions
 - **lui** – Load Upper Immediate
 - **auipc** – Add Upper Immediate to PC



Lighting Up LUI

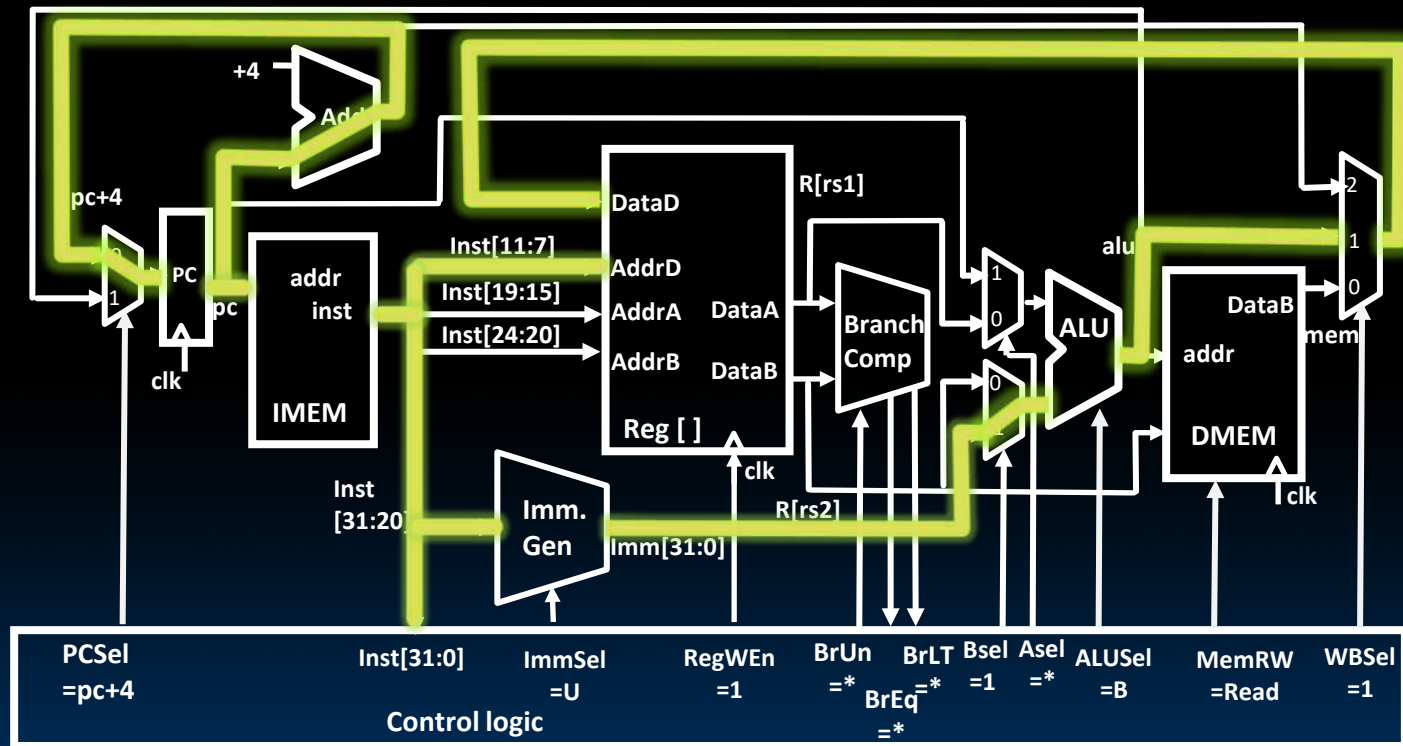


Lighting Up AUIPC

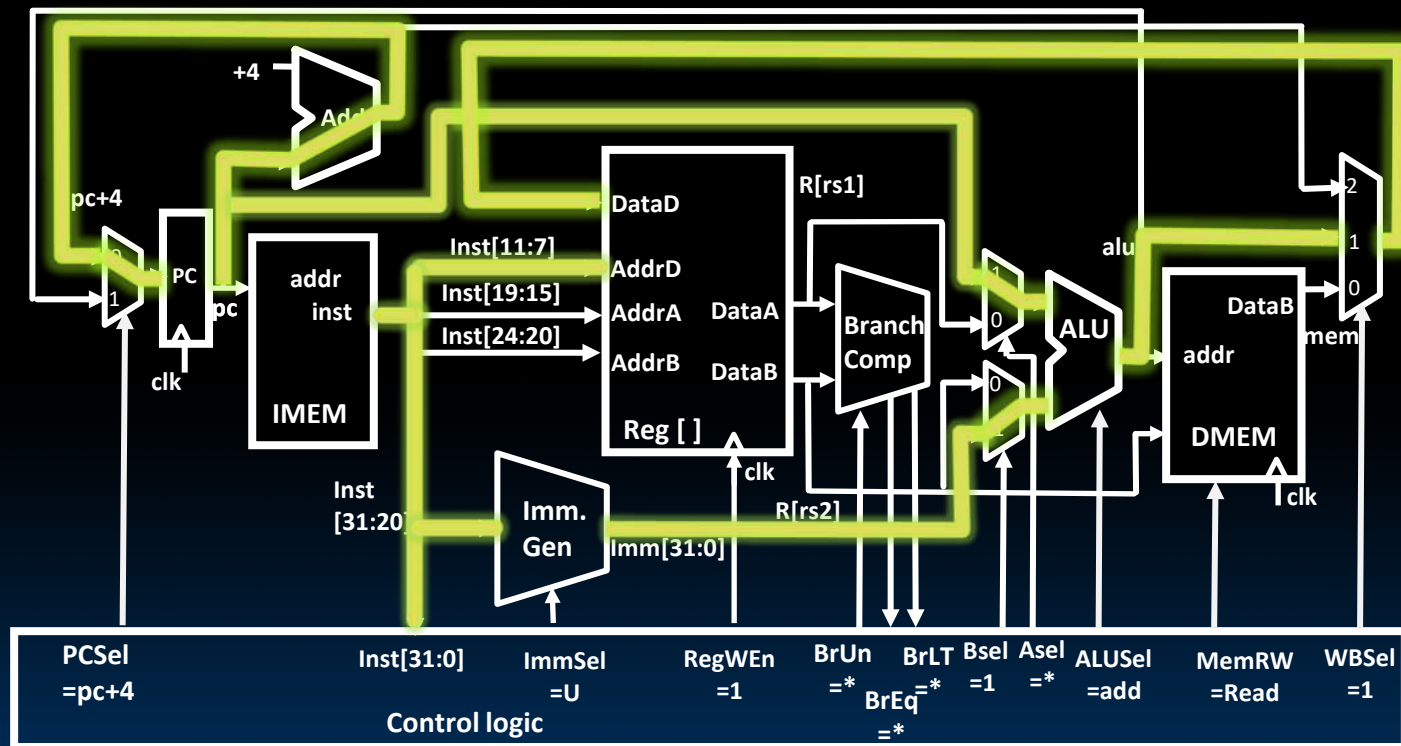

**“And In
Conclusion...”**

Complete RV32I Datapath!

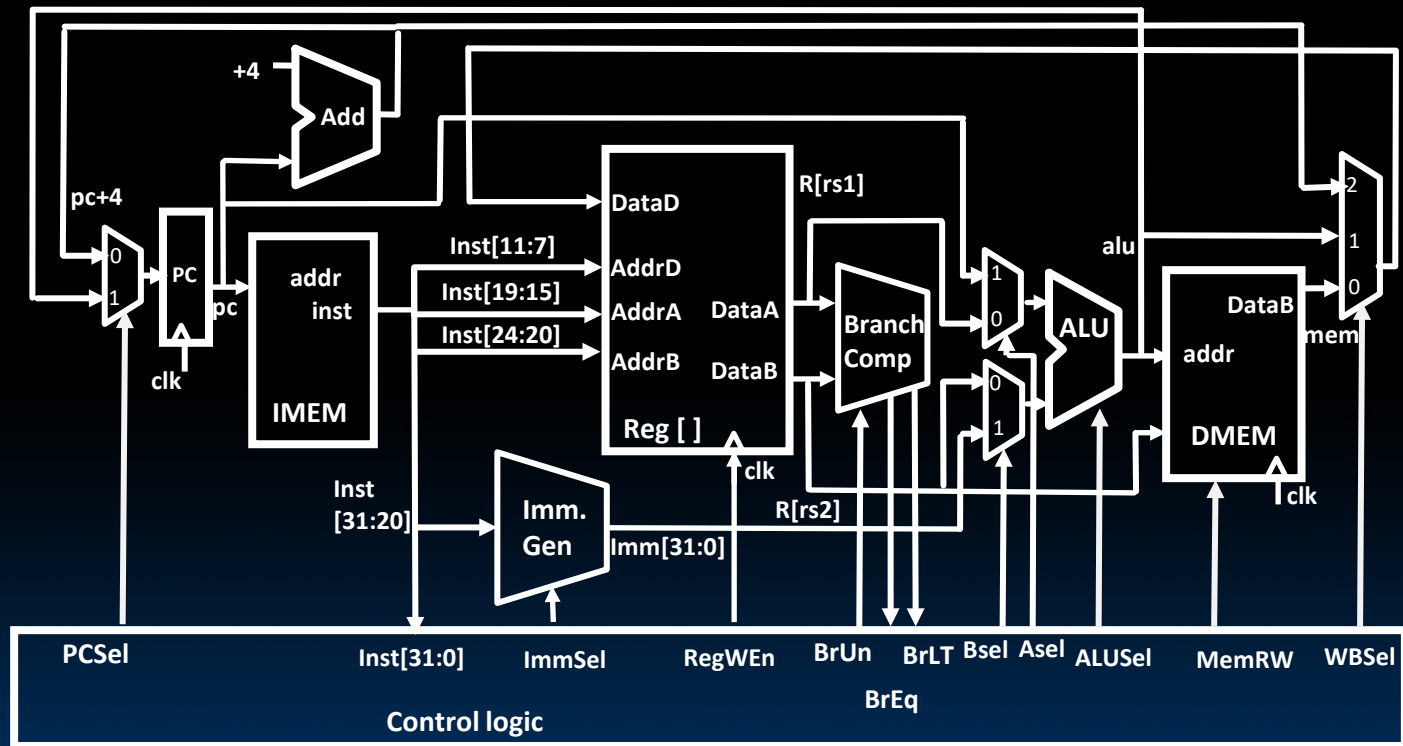



Complete RV32I ISA!

Open RISC-V Reference Card

Base Integer Instructions: RV32I							
Category	Name	Fmt	RV32I Base	Category	Name	Fmt	RV32I Base
Shifts	Shift Left Logical	R	SLL rd,rs1,rs2	Loads	Load Byte	I	LB rd,rs1,imm
	Shift Left Log. Imm.	I	SLLI rd,rs1,shamt		Load Halfword	I	LH rd,rs1,imm
	Shift Right Logical	R	SRL rd,rs1,rs2		Load Byte Unsigned	I	LBU rd,rs1,imm
	Shift Right Log. Imm.	I	SRLI rd,rs1,shamt		Load Half Unsigned	I	LHU rd,rs1,imm
	Shift Right Arithmetic	R	SRA rd,rs1,rs2		Load Word	I	LW rd,rs1,imm
	Shift Right Arith. Imm.	I	SRAI rd,rs1,shamt	Stores	Store Byte	S	SB rs1,rs2,imm
Arithmetic	ADD	R	ADD rd,rs1,rs2		Store Halfword	S	SH rs1,rs2,imm
	ADD Immediate	I	ADDI rd,rs1,imm	Branches	Store Word	S	SW rs1,rs2,imm
	SUBtract	R	SUB rd,rs1,rs2		Branch =	B	BEQ rs1,rs2,imm
	Load Upper Imm	U	LUI rd,imm		Branch ≠	B	BNE rs1,rs2,imm
	Add Upper Imm to PC	U	AUIPC rd,imm		Branch <	B	BLT rs1,rs2,imm
	XOR	R	XOR rd,rs1,rs2		Branch ≥	B	BGE rs1,rs2,imm
Logical	XOR Immediate	I	XORI rd,rs1,imm		Branch < Unsigned	B	BLTU rs1,rs2,imm
	OR	R	OR rd,rs1,rs2		Branch ≥ Unsigned	B	BGEU rs1,rs2,imm
	OR Immediate	I	ORI rd,rs1,imm	Jump & Link	J&L	J	JAL rd,imm
	AND	R	AND rd,rs1,rs2		Jump & Link Register	I	JALR rd,rs1,imm
	AND Immediate	I	ANDI rd,rs1,imm	Synch	Synch thread	I	FENCE
	Compare Set <	R	SLT rd,rs1,rs2				
Compare	Set < Immediate	I	SLTI rd,rs1,imm				
	Set < Unsigned	R	SLTU rd,rs1,rs2	Environment	CALL	I	ECALL
	Set < Imm Unsigned	I	SLTIU rd,rs1,imm		BREAK	I	EBREAK

Not in
61C

- We have designed a complete datapath
 - Capable of executing all RISC-V instructions in one cycle each
 - Not all units (hardware) used by all instructions
- 5 Phases of execution
 - IF, ID, EX, MEM, WB
 - Not all instructions are active in all phases
- Controller specifies how to execute instructions
 - We still need to design it